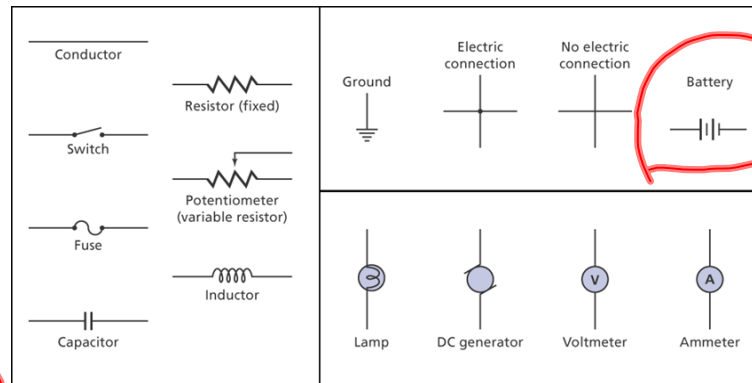


Diagramming Circuits

An electric circuit is drawn using standard symbols for the circuit elements.

Such a diagram is called a circuit schematic. Some of the symbols used in circuit schematics are shown below.



Pg. 599


Drawing Schematic Diagrams

May 31-11:55 AM

A 30.0-V battery is connected to a 10.0- Ω resistor.


Draw a circuit containing a battery, an ammeter, and a resistor.

Show the direction of the conventional current.

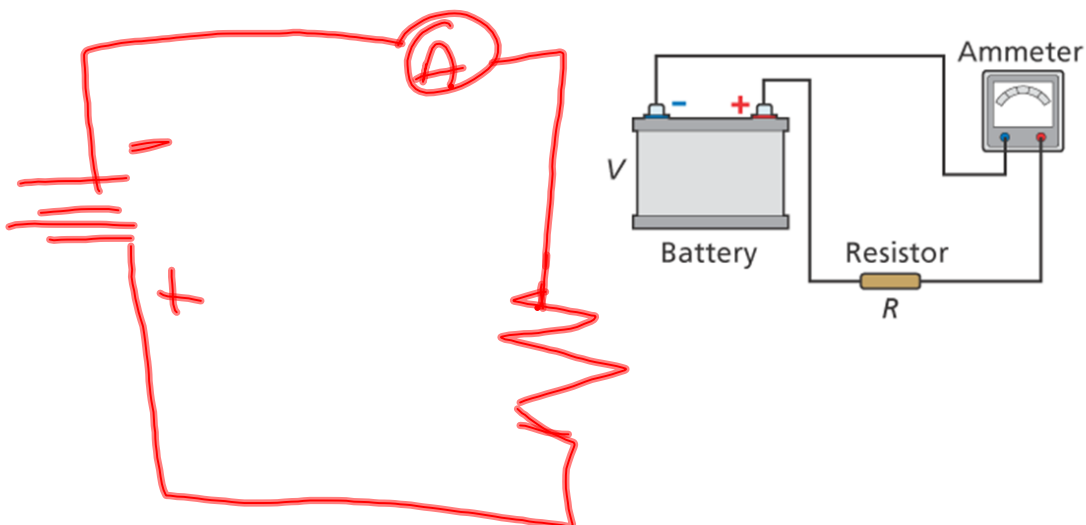

May 31-11:58 AM

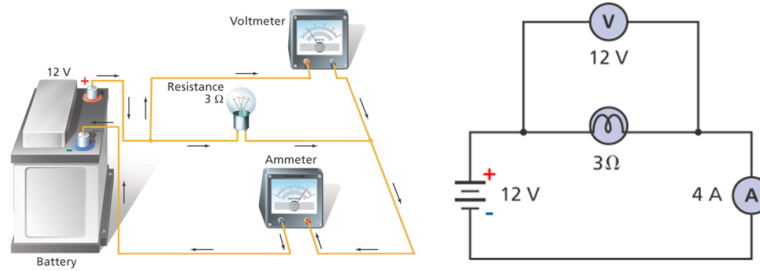An artist's drawing and a schematic of the same circuit are shown below.




An ammeter measures current and a voltmeter measures potential differences. Each instrument has two terminals, usually labeled + and -. A voltmeter measures the potential difference across any component of a circuit. When connecting the voltmeter in a circuit, always connect the + terminal to the end of the circuit component that is closer to the positive terminal of the battery, and connect the - terminal to the other side of the component.

When a voltmeter is connected across another component, it is called a **parallel connection** because the circuit component and the voltmeter are aligned parallel to each other in the circuit, as diagrammed in the figure.


May 31-12:00 PM

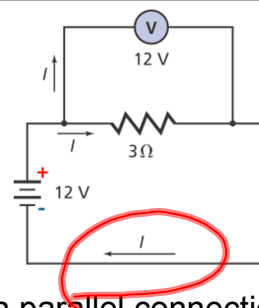Any time the current has two or more paths to follow, the connection is labeled *parallel*. The potential difference across the voltmeter is equal to the potential difference across the circuit element.



Always associate the words voltage across with a parallel connection.

An ammeter measures the current through a circuit component. The same current going through the component must go through the ammeter, so there can be only one current path. A connection with only one current path is called a **series connection**.

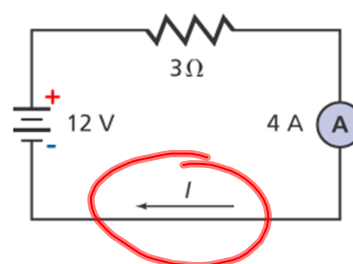

May 31-12:56 PM

To add an ammeter to a circuit, the wire connected to the circuit component must be removed and connected to the ammeter instead.


Then, another wire is connected from the second terminal of the ammeter to the circuit component.

In a series connection, there can be only a single path through the connection.

~~Always associate the words *current through* with a series connection.~~

Ex: 1

Draw a circuit diagram with a resistor, ammeter, and battery. Connect the ammeter in series with the other two components.

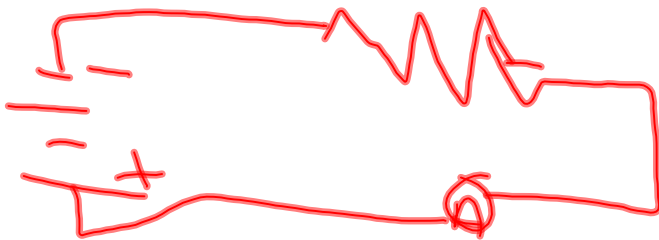

May 31-12:59 PM

No clickers & yes calculators!!


Have out the 22.1 Diagramming Circuit notes.

Do the last two examples!!

Jun 2-8:07 AM

Ex: 2

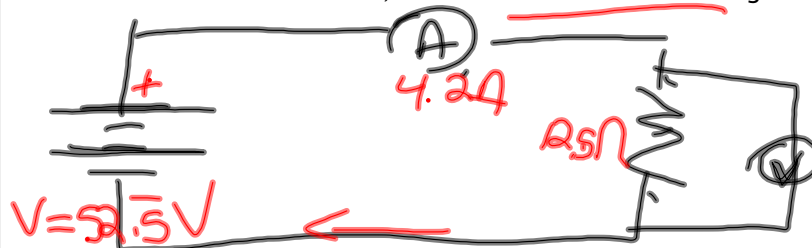Draw a circuit diagram with a resistor, ammeter, and battery. Add a voltmeter to measure potential difference across the resistors. If the ammeter reads 4.2 A and the resistor is $12.5\ \Omega$, indicate the voltmeter reading.



Ex: 3

Draw a circuit diagram with a lamp, on-off switch, and battery. Add a voltmeter and an ammeter across the lamp.



May 31-1:05 PM

① Study

② Vocab Quiz

③ Pg. 600

12-1 bulb

④ 22.1 Study Guide

Jun 2-12:15 PM