

## CHAPTER

## 22

## Study Guide

## Current Electricity

## Vocabulary Review

Write the term that correctly completes the statement. Use each term once.

ampere

electric current

resistor

battery

kilowatt-hour

series connection

conventional current

parallel connection

superconductor

electric circuit

resistance

1. \_\_\_\_\_ A(n) \_\_\_\_\_ is a material with zero resistance.
2. \_\_\_\_\_ The \_\_\_\_\_ of a wire determines how much current will flow through the wire when a voltage is applied.
3. \_\_\_\_\_ The \_\_\_\_\_ is the flow of charged particles.
4. \_\_\_\_\_ In a(n) \_\_\_\_\_, there is only one path for the current.
5. \_\_\_\_\_ A(n) \_\_\_\_\_ is a unit of energy.
6. \_\_\_\_\_ In a(n) \_\_\_\_\_, there is more than one path for the current.
7. \_\_\_\_\_ A(n) \_\_\_\_\_ is the unit of current.
8. \_\_\_\_\_ A(n) \_\_\_\_\_ is a closed loop in which electrons can move.
9. \_\_\_\_\_ A(n) \_\_\_\_\_ converts chemical energy to electrical energy.
10. \_\_\_\_\_ A(n) \_\_\_\_\_ is the flow of positive charge.
11. \_\_\_\_\_ A(n) \_\_\_\_\_ is a device designed to have a specific resistance.

## Section 22.1

## Current and Circuits

In your textbook, read about electric circuits on pages 591–593.

For each statement below, write true or rewrite the italicized part to make the statement true.

1. \_\_\_\_\_ *Negative* charge flows from a higher potential to a lower potential.
2. \_\_\_\_\_ The flow of *electrons* is called conventional current.

**22 Study Guide***continued*

3. \_\_\_\_\_ The total charge passing through a point on a circuit is the current multiplied by the *time* the charge flows.
4. \_\_\_\_\_ Electrical energy is converted into kinetic energy in a *generator*.
5. \_\_\_\_\_ The number of *electrons* in a closed circuit does not change.

*Write the term that correctly completes the statement.*

A circuit includes a (6) \_\_\_\_\_, which increases the potential energy of the charge, and a device that (7) \_\_\_\_\_ the potential energy of the charge.

The potential energy lost by the charges is usually converted into another form of

- (8) \_\_\_\_\_. For example, a lamp converts electrical energy to  
 (9) \_\_\_\_\_ energy.

*Read the passage below to answer questions 10–13.*

**A closed circuit consists of a battery of constant voltage connected to a heater with wires. Electrons are flowing through the circuit, causing the heater to emit thermal energy.**

10. Draw a sketch of the circuit.

11. What do the battery and the heater do to the electrons?

---



---



---

12. What does the law of conservation of electric charge state?

---

13. Is it possible for the current leaving the heater to be different than the current entering the heater? Why or why not?

---



---



---



**22 Study Guide***continued*

- 27.** For a wire that obeys Ohm's law, the resistance of a wire depends on the \_\_\_\_\_ the wire.
- a.** current in
  - b.** length of
  - c.** power delivered by
  - d.** voltage across
- 28.** If a  $200\text{-}\Omega$  resistor is connected to a  $5\text{-V}$  battery, the current in the circuit will be \_\_\_\_\_.
- a.**  $0.025\text{ A}$
  - b.**  $2.5\text{ A}$
  - c.**  $40\text{ A}$
  - d.**  $1000\text{ A}$
- 29.** A device that can be used to change the current in a circuit in a continuous way is a \_\_\_\_\_.
- a.** potentiometer
  - b.** battery
  - c.** motor
  - d.** lamp

*Answer the following questions.*

- 30.** Draw a circuit diagram with a resistor, ammeter, and battery. Connect the ammeter in series with the other two components.
- 31.** Draw a circuit diagram with a resistor, battery, and voltmeter. Connect the voltmeter in parallel across the resistor. Draw another circuit diagram showing the voltmeter connected in parallel across the battery.